


CS 272 - Fall 2017

Homework 5

Due: Wednesday, November 15

Do the following questions pertaining to BJTs covered in Chapter 22 of the book and lecture notes.
Submit your answers on paper in class.

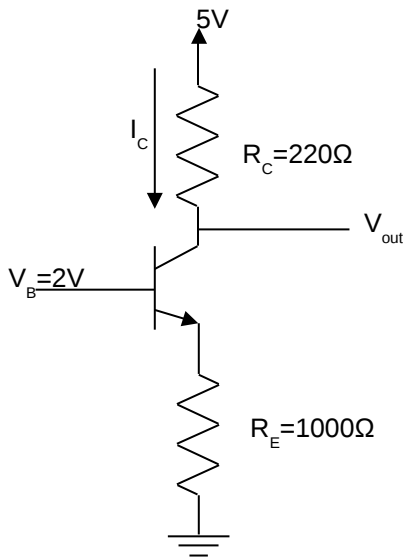- 1) Given the circuit below, with various voltages shown, compute the values of I_C , and V_{out} . Show your work.



2) Give the truth table for the following CMOS circuit.

